

Lab 4: Seven-segment display decoder

Preparation tasks

Nexys A7 anode table

- 7-seg displays have common anode each.
- Logic 0 value allows the current to flow through a transistor to 7-seg display.
- Logic 1 value prevents the current to flow through a transistor to 7-seg display.
- In the DISPLAY column, the value 0 means rightmost and 7 means leftmost.

AND	PIN	DISPLAY
AN0	J17	0
AN1	J18	1
AN2	T9	2
AN3	J14	3
AN4	P14	4
AN5	T14	5
AN6	K2	6
AN7	U13	7

Nexys A7 cathode table

- Logic 0 value allows the current to flow through the LEDs in 7-seg display.
- Logic 1 value prevents the current to flow through the LEDs in 7-seg display.

CTD	PIN
CA	T10

CTD	PIN
CB	R10
CC	K16
CD	K13
CE	P15
CF	T11
CG	L18
DP	H15

Decoder truth table

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1

Hex	Inputs	A	B	C	D	E	F	G
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

Seven-segment display decoder

VHDL architecture from source file hex_7seg.vhd

```

architecture Behavioral of hex_7seg is

begin

    -----
    -- p_7seg_decoder:
    -- A combinational process for 7-segment display decoder.
    -- Any time "hex_i" is changed, the process is "executed".
    -- Output pin seg_o(6) corresponds to segment A, seg_o(5) to B, etc.
    -----
    p_7seg_decoder : process(hex_i)
    begin
        case hex_i is
            when "0000" =>
                seg_o <= "0000001";    -- 0
            when "0001" =>
                seg_o <= "1001111";    -- 1

            -- WRITE YOUR CODE HERE
            when "0010" =>
                seg_o <= "0010010";    -- 2
            when "0011" =>
                seg_o <= "0000110";    -- 3
            when "0100" =>
                seg_o <= "1001100";    -- 4
            when "0101" =>
                seg_o <= "0100100";    -- 5
            when "0110" =>
                seg_o <= "0100000";    -- 6
            when "0111" =>
                seg_o <= "0001111";    -- 7
            when "1000" =>

```

```

        seg_o <= "0000000";    -- 8
    when "1001" =>
        seg_o <= "0000100";    -- 9
    when "1010" =>
        seg_o <= "0001000";    -- A
    when "1011" =>
        seg_o <= "1100000";    -- b
    when "1100" =>
        seg_o <= "0110001";    -- C
    when "1101" =>
        seg_o <= "1000010";    -- d
    when "1110" =>
        seg_o <= "0110000";    -- E
    when others =>
        seg_o <= "0111000";    -- F
    end case;
end process p_7seg_decoder;

end Behavioral;

```

VHDL stimulus process from testbench file tb_hex_7seg.vhd

```

p_stimulus : process
begin
    -- Report a note at the begining of stimulus process
    report "Stimulus process started" severity note;

    -- First test values
    s_hex <= "0000"; wait for 100 ns;

    -- WRITE OTHER TESTS HERE
    s_hex <= "0001"; wait for 100 ns;
    s_hex <= "0010"; wait for 100 ns;
    s_hex <= "0011"; wait for 100 ns;
    s_hex <= "0100"; wait for 100 ns;
    s_hex <= "0101"; wait for 100 ns;
    s_hex <= "0110"; wait for 100 ns;
    s_hex <= "0111"; wait for 100 ns;
    s_hex <= "1000"; wait for 100 ns;
    s_hex <= "1001"; wait for 100 ns;
    s_hex <= "1010"; wait for 100 ns;
    s_hex <= "1011"; wait for 100 ns;
    s_hex <= "1100"; wait for 100 ns;
    s_hex <= "1101"; wait for 100 ns;

```


```

s_hex <= "1110"; wait for 100 ns;
s_hex <= "1111"; wait for 100 ns;

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Simulated time waveforms

 

VHDL code from source file top.vhd with 7-segment module instantiation

```

-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
  port map(
    hex_i    => SW,
    seg_o(6) => CA,

    -- WRITE YOUR CODE HERE
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
  );

```

LED(7:4) indicators

Truth table

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0

Hex	Inputs	LED4	LED5	LED6	LED7
1	0001	0	0	1	1
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

VHDL code for LEDs(7:4)

```
-- LED(7:4) indicators
-- Turn LED(4) on if input value is equal to 0, ie "0000"
-- WRITE YOUR CODE HERE
LED(4) <= '1' when (SW = "0000") else
    '0';

-- Turn LED(5) on if input value is greater than "1001", ie 9
-- WRITE YOUR CODE HERE
LED(5) <= (SW(3) and SW(1)) or (SW(3) and SW(2));

-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
-- WRITE YOUR CODE HERE
```

```

LED(6) <= SW(0);

-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
-- WRITE YOUR CODE HERE
LED(7) <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or SW = "1000")
else
    '0';

```

Simulated time waveforms

