

LAB01 - Gates

Link to my GitHub repository

<https://github.com/xruine00/Digital-electronics-1>

De Morgan's laws

Equations for the implementation of gates:

$$f(c, b, a) = \bar{b}a + \bar{c}\bar{b}$$


$$f(c, b, a)_{\text{NAND}} = \overline{\bar{b}a \cdot \bar{c}\bar{b}}$$

$$f(c, b, a)_{\text{NOR}} = \overline{b + \bar{a} + c + \bar{b}}$$

The truth table:

c	b	a	f(c,b,a)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Screenshot with time waveforms:

 

Defined functions in VHDL:

```

library ieee;                -- Standard library
use ieee.std_logic_1164.all; -- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----

entity gates is
  port(
    a_i    : in  std_logic;    -- Data input
    b_i    : in  std_logic;    -- Data input
    c_i    : in  std_logic;    -- Data input
    f_o    : out std_logic;    -- output function
    fnand_o : out std_logic;    -- NAND output function
    fnor_o  : out std_logic    -- NOR output function
  );
end entity gates;

-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
  f_o    <= ((not b_i) and a_i) or ((not c_i) and (not b_i));
  fnand_o <= ((b_i nand b_i) nand a_i) nand ((c_i nand c_i) nand (b_i nand
b_i));
  fnor_o  <= ((b_i nor (a_i nor a_i)) nor (c_i nor b_i)) nor ((b_i nor (a_i nor
a_i)) nor (c_i nor b_i));

end architecture dataflow;

```

Link to the EDA Playground:

<https://www.edaplayground.com/x/ezmf>

Distributive laws

Equations for the implementation of gates:

$$f1 = x \cdot y + x \cdot z$$

$$f2 = x \cdot (y + z)$$

$$f3 = (x + y) \cdot (x + z)$$

$$f4 = x + (y \cdot z)$$

$$f(1) = f(2) \rightarrow x \cdot y + x \cdot z = x \cdot (y + z)$$

$$f(3) = f(4) \rightarrow (x + y) \cdot (x + z) = x + (y \cdot z)$$


The truth table for f1 and f2:

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

The truth table for f3 and f4:

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Screenshot with time waveforms:

 

Defined functions in VHDL:

```
library ieee;                -- Standard library
use ieee.std_logic_1164.all;-- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----

entity gates is
  port(
    x_i    : in  std_logic;      -- Data input
    y_i    : in  std_logic;      -- Data input
    z_i    : in  std_logic;      -- Data input
    f1_o    : out std_logic;      -- Function 1
    f2_o    : out std_logic;      -- Function 2
    f3_o    : out std_logic;      -- Function 3
    f4_o    : out std_logic;      -- Function 4
  );
end entity gates;

-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
  f1_o <= (x_i and y_i) or (x_i and z_i);
  f2_o <= x_i and (y_i or z_i);
  f3_o <= (x_i or y_i) and (x_i or z_i);
  f4_o <= x_i or (y_i and z_i);

end architecture dataflow;
```

Link to the EDA Playground:

https://www.edaplayground.com/x/GG_2